

Design Procedure

1. Specification

- Write a specification for the circuit if one is not already available

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification

3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

4. Technology Mapping

- Map the logic diagram or netlist to the implementation technology selected

5. Verification

- Verify the correctness of the final design

Design Example

1. Specification

- BCD to Excess-3 code converter
- Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits
- BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word
- Implementation:
 - multiple-level circuit
 - NAND gates (including inverters)

Design Example (continued)

1. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table
- Variables
 - BCD:
A,B,C,D
- Variables
 - Excess-3
W,X,Y,Z
- Don't Cares
 - BCD 1010 to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1

Design Example (continued)

1. Optimization

- a. 2-level using K-maps

$$W = A + BC + BD$$

$$X = B'C + B'D + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$

 
 
 
 


Fig. 3-10 Maps for BCD-to-Excess-3 Code Converter

Design Example (continued)

1. Optimization (continued)

a. Multiple-level using transformations

$$W = A + BC + BD$$

$$X = B'C + B'D + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$

$$G = 7 + 10 + 6 + 0 = 23$$

– Perform extraction, finding factor:

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = B'T_1 + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$

$$G = 2 + 4 + 7 + 6 + 0 = 19$$

Design Example (continued)

1. Optimization (continued)

- a. Multiple-level using transformations

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = B'T_1 + BC'D'$$

$$Y = CD + C'D'$$

$$Z = D'$$

$$G = 19$$

- An additional extraction not shown in the text since it uses a Boolean transformation: ($C'D' = (C + D)' = T_1'$):

$$W = A + BT_1$$

$$X = B'T_1 + BT_1'$$

$$Y = CD + T_1'$$

$$Z = D'$$

$$G = 2 + 4 + 6 + 4 + 0 = 16$$

Design Example (continued)

1. Technology Mapping

- Mapping with a library containing inverters and 2-input NAND, 2-input NOR, and 2-2 AOI gates

